

wednesday:

1st / June / 2021

① Arduino:

- two types of Arduino
 - clone Arduino → Arduino Uno.
- 13 digital pins. (output) (led, led, relay, etc)
- 6 Analog pins to connect inputs (sensors)
- 4 pins (power supply for input and output).
- power jack (for power supply)
- USB port to upload program.
- Reset button.

② Software: (case sensitive.)

#define → define pins with variable
define led1 13 → pin
↓
variable.


void setup()

{ → define pin as output or input
using pinMode(), (13, output)

void loop()

{ → Main program
} → Commands and logic of what to do?
digitalWrite (led1, HIGH);

1 16

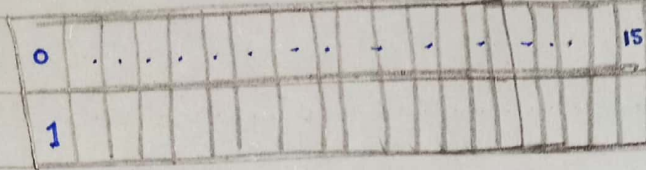

lcd.setCursor(5,1)

lcd.print("a")

16 * 2 LCD Module.

→ 16 Columns.

→ 2 Rows.

→ total 32 Characters:

1 → V_{SS} (Ground) → GND

2 → V_{DD} (5V) → 5V

3 → V_E (contrast) → Resistor (1k ohm)

4 → R_S (Register Select) → Digital pin of arduino.

5 → R_W (Read/Write) for write (low) for read (high).

6 → (Enable) → digital Pin of Arduino.

7 → D₀

8 → D₁

9 → D₂

10 → D₃

11 → D₄

12 → D₅

13 → D₆

14 → D₇


→ digital pin of Arduino.

15 → Backlight Cathode → 5V

16 → Backlight Anode → Gnd.

Forwarded	H	L	H	L	→
Backward	L	H	L	H	
Left	L	L	H	L	→ only right motor work
Right	H	L	L	L	→ only left motor work

① What is an Ultrasonic Sensor?

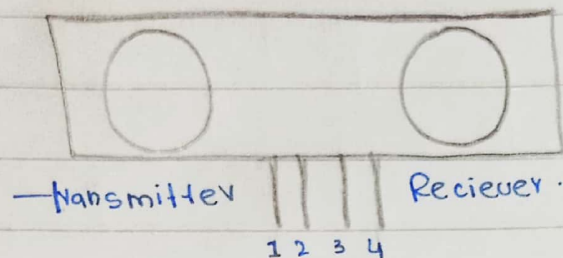

1 → 5V → Vcc

2 → Trig → Digital pin of arduino (output)

3 → Echo → " " " " (Input)

4 → Gnd.


① Why we use motor driver IC?

In 3	In 4	motor 2
low	High	forward
High	low	Backward
		forward

Arduino → output → 5V → motor working

no 9V to 12 that why we use motor driver IC.

left side on if high

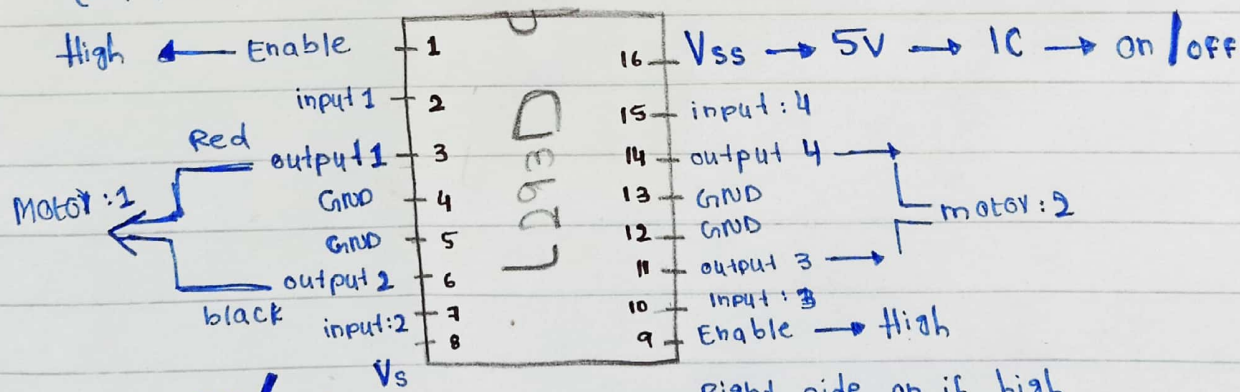

9V/12V

Battery ka negative GND mea.

Right side on if high

Input 1	Input 2	Motor 1
High	low	forward
low	High	Backward